

Scan Latch  
Laboratory 2  
ECE 426/526  
11 February 2007

Laboratory 2 builds upon Laboratory 1 with the design of common cell that supports scan testing of digital integrated circuits. The cell uses the laboratory D-latch (master) adding combinational logic multiplexor to this D-input, and a second D-latch (slave).

Each standard cell has a data-sheet with a cell description, logic equations, truth table, performance characteristics, schematic and polygon layout. This data-sheet is the basis of laboratory reports.


A report template of the data-sheet is completed and submitted for each cell. The "Standard Cell Report Template" is located at

[http://ece.pdx.edu/~daasch/course/x25/lab/Full\\_Datasheet.doc](http://ece.pdx.edu/~daasch/course/x25/lab/Full_Datasheet.doc)

The goals for this laboratory are

- Build upon understanding of CMOS circuits and systems
- Select a CMOS design of a scan master-slave
- Create a schematic and physical layout of selection
- Verify function of schematic and physical layout
- Modify prototype to meet specifications
- Document final design

 It is recommended that you use a the base the same latch that your team selected for Laboratory 1.



A drive inverter (output buffer) for  $Q$  is recommended.

Design logic and physical design of CMOS Scan Master-Slave for an external output load capacitor equal to FO4.

Label the inputs "DIN", "TI" test input, "TE" test enable, "CLK" and "CLKBAR" and the output "Q".

Include both types of ohmic contacts to the physical design.

All transistors should be minimum length.

Test enable is active high  $TE=1$  for storing the data from signal  $TI$ . Test enable low  $TE=0$  for storing the data from signal  $DIN$ .

Complete the following components of the data-sheet template for scan master-slave standard cell.

Cell Description, Cell Symbol, Cell Truth Table, Cell Schematic Diagram, Cell Layout

Performance Analysis; Q (only) rise and fall, propagation tables for DIN to Q (only) and TI to Q (only), and propagation equations for these data to output paths.

Add a table summarizing the latch setup and latch hold times.