



Figure 16.3: Lab 6 complete circuit.